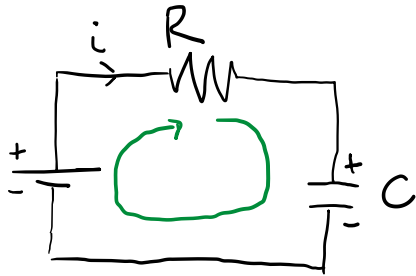


# RC Circuits

Derive the solutions for the charge, voltage, and current of a capacitor in a simple RC circuit.



$$i \equiv \frac{dq}{dt}$$

From KLR

$$\varepsilon - iR - \frac{q}{C} = 0$$

$$\Rightarrow \varepsilon - \frac{dq}{dt}R - \frac{q}{C} = 0 \Rightarrow \frac{dq}{dt}R = \varepsilon - \frac{q}{C} \Rightarrow \frac{dq}{dt} \left( \frac{R}{\varepsilon - \frac{q}{C}} \right) = 1$$

$$\int_0^{q(t)} \frac{1}{\frac{\varepsilon}{R} - \frac{q}{RC}} \frac{dq}{dt} dt = \int_0^t 1 dt$$

$$u = \frac{\varepsilon}{R} - \frac{q}{RC} \quad du = -\frac{dq}{RC}$$

$$\Rightarrow \int_{\frac{\varepsilon}{R}}^{\frac{\varepsilon}{R} - \frac{q(t)}{RC}} \frac{-RC du}{u} = \int_0^t dt$$


$$\Rightarrow -RC \ln |u| \Big|_{\frac{\varepsilon}{R}}^{\frac{\varepsilon}{R} - \frac{q(t)}{RC}} = t \Rightarrow \ln \left| \frac{\frac{\varepsilon}{R} - \frac{q(t)}{RC}}{\frac{\varepsilon}{R}} \right| = -\frac{t}{RC} \Rightarrow 1 - \frac{q(t)}{C\varepsilon} = e^{-\frac{t}{RC}}$$

$$\boxed{q(t) = C\varepsilon(1 - e^{-\frac{t}{RC}})}$$

$$i(t) = \frac{dq(t)}{dt} = -\cancel{C\varepsilon} \left( -\frac{1}{RC} \right) e^{-\frac{t}{RC}} = \boxed{\frac{\varepsilon}{R} e^{-\frac{t}{RC}}}$$

$$V_C(t) = \frac{q}{C} = \frac{C\varepsilon(1 - e^{-\frac{t}{RC}})}{C} = \boxed{\varepsilon(1 - e^{-\frac{t}{RC}})}$$

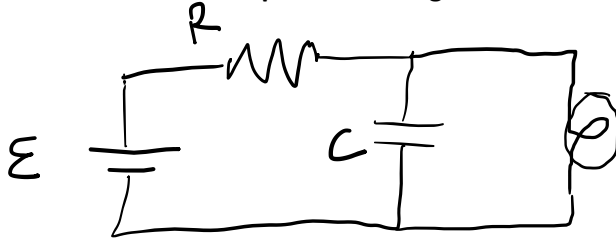A circuit is designed with a battery and a variable resistor in series with a capacitor and lightbulb, which are connected in parallel. A diagram is shown below...



A multi-meter measures the voltage across the capacitor over time. Sketch a graph of this behavior, and explain each trend.

