

Kirchhoff's Laws and Capacitors

Three capacitors of equal capacitance are arranged in a circuit in parallel with the only other element in the circuit: a battery with emf of 5V. What is the charge on each of the capacitor plates? Suppose one of these capacitors is removed. What happens to the charge on each plate?

Derive the capacitance of a conducting spherical shell.