

## 2-22-2019: Resistance, KCL, and KRL

Friday, February 22, 2019 9:02 AM

Let's review what we learned last time...

$$V = iR, \quad \vec{E} = \rho \vec{j}$$

$$P = \frac{dU}{dt} = iV = i^2 R = \frac{V^2}{R}$$

$$R_{eq} = \sum_{i=1}^n R_i \quad (\text{for "n" resistors in-series})$$

Kirchhoff's Loop Rule:




resistors: following  $i$   $-iR$   
against  $i$   $+iR$

emf:  $'+' \text{ to } '-'$   $-\mathcal{E}$

$'-' \text{ to } '+'$   $+\mathcal{E}$

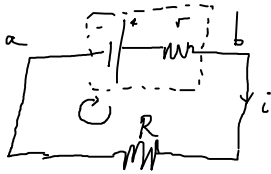Last time, we looked at a non-ideal emf generator. What would be the current through the following system?



KLR:  $+\mathcal{E} - ir - iR = 0$

$$i_a = \frac{\mathcal{E}}{r+R}$$

Ohm:


$$i_a = \frac{\mathcal{E}}{R_{eq}} = \frac{\mathcal{E}}{r+R}$$

What's the potential drop across the non-ideal battery?

$$V_a + \mathcal{E} - ir = V_b$$

$$V_b - V_a = \mathcal{E} - ir$$

$$\boxed{V_{ba} = \mathcal{E} - ir}$$

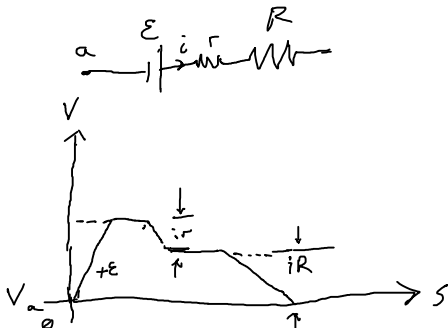


What is the power dissipated by each element?

$$P_E = i \mathcal{E}$$

$$P_r = i^2 r \neq \frac{\mathcal{E}^2}{r}$$

$$P_R = i^2 R \neq \frac{\mathcal{E}^2}{R}$$

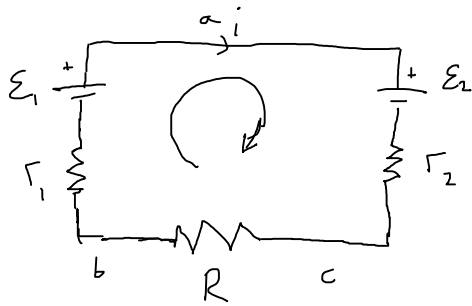What is the current in the circuit below?




KLR

$$-\mathcal{E}_2 - i r_2 - i R - i r_1 + \mathcal{E}_1 = 0$$

$$i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R + r_1 + r_2}$$

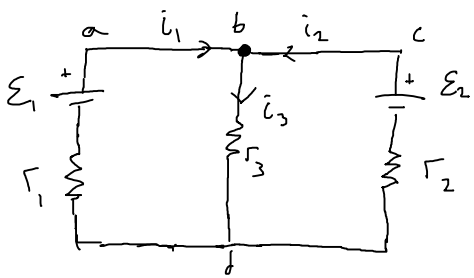Suppose the above circuit had a junction in the center like below...




At point b, we can make use of another of Kirchhoff's rules: Kirchhoff's Current Rule...

KCL

$$i_1 + i_2 = i_3$$

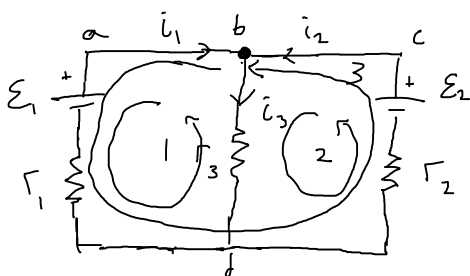Let's now apply KRL to this system by using three loops...



KRL

$$1 \quad \mathcal{E}_1 + i_3 R_3 + i_1 R_1 = 0$$

$$2 \quad \mathcal{E}_2 + i_2 R_2 + i_3 R_3 = 0$$


$$3 \quad -\mathcal{E}_1 + \mathcal{E}_2 + i_2 R_2 - i_1 R_1 = 0$$

Notice that the third result is the sum of the smaller two loops (the KRL solution is a superposition of loops 1 and 2).

Let's take a look at a circuit that with resistors in parallel...

i i i

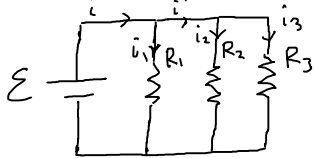Let's take a look at a circuit that with resistors in parallel...



$$V_1 = V_2 = V_3 = \mathcal{E}$$

$$i_1 R_1 = i_2 R_2 = i_3 R_3 = \mathcal{E}$$

$$i' = i_2 + i_3$$

$$i = i' + i_1 = i_1 + i_2 + i_3 = \frac{\cancel{\mathcal{E}}}{R_1} + \frac{\cancel{\mathcal{E}}}{R_2} + \frac{\cancel{\mathcal{E}}}{R_3} = \frac{\cancel{\mathcal{E}}}{R_{eq}}$$

$$\Rightarrow \frac{1}{R_{eq}} = \sum_i^n \frac{1}{R_i}$$