

Ohm's Law and Kirchhoff's Voltage Rule


Using the observation that electric field in a conductor is proportional to current density (a.k.a. Ohm's Law), can you derive the formula $V=IR$?

OHM'S LAW SAYS THAT $\vec{j} \propto \vec{E}$.

$$\Rightarrow \vec{j} = \sigma \vec{E}$$

↑
CONDUCTIVITY.

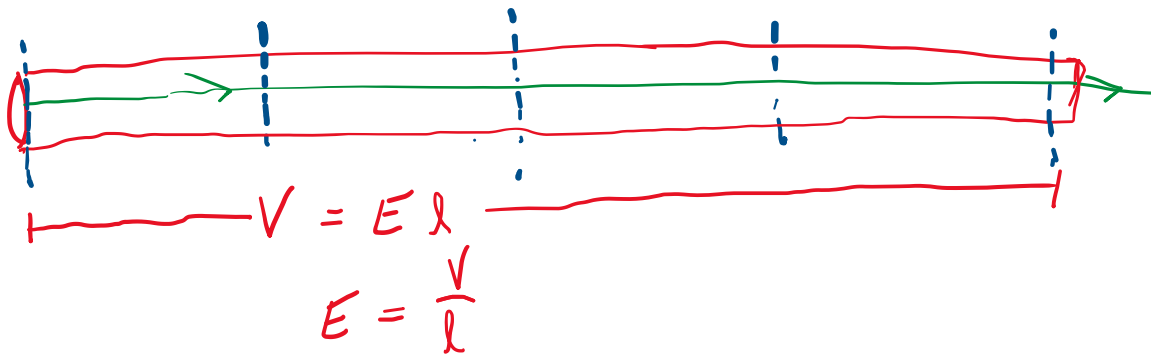IN A CLASSICAL WIRE, FIELD POTENTIAL LINES ARE LIKE SO - - -



WE ALSO KNOW THAT CURRENT DENSITY IS RELATED TO CURRENT AS FOLLOWS. - -

$$\vec{j} = \frac{i}{A} \quad \text{So, } \vec{j} = \sigma \vec{E} \Rightarrow \frac{i}{A} = \sigma \left(\frac{V}{l} \right). \quad \vec{A} \parallel \vec{l}.$$

$$\text{So, } i l = \sigma A V \Rightarrow V = i \left(\frac{l}{\sigma A} \right). \quad \sigma \equiv \frac{1}{\rho}.$$

$$\Rightarrow V = i \left(\frac{\rho l}{A} \right). \quad R \equiv \frac{\rho l}{A} \Rightarrow \boxed{V = i R}$$

Suppose I have two wires:

- one has a radius of $r_1 = 0.100 \text{ m}$, a length of $l_1 = 0.100 \text{ m}$, and a resistivity of $\rho_1 = 5.00 \Omega \cdot \text{m}$.
- a second wire has a radius of $r_2 = 0.200 \text{ m}$, a length of $l_2 = 0.190 \text{ m}$, and a resistivity of $\rho_2 = 5.30 \Omega \cdot \text{m}$.

Which wire has a greater resistivity? Which has a greater resistance?


- THE SECOND WIRE HAS A GREATER RESISTIVITY ($\rho_2 > \rho_1$).

$$R_1 = \frac{\rho_1 l_1}{A_1} = \frac{\rho_1 l_1}{\pi r_1^2} = \frac{(5.00 \Omega \cdot \text{m})(0.100 \text{ m})}{\pi (0.100 \text{ m})^2} = 15.9 \Omega$$

$$R_2 = \frac{\rho_2 l_2}{A_2} = \frac{\rho_2 l_2}{\pi r_2^2} = \frac{(5.30 \Omega \cdot \text{m})(0.190 \text{ m})}{\pi (0.200 \text{ m})^2} = 8.01 \Omega$$

- THE FIRST WIRE HAS A GREATER RESISTANCE ($R_1 > R_2$)

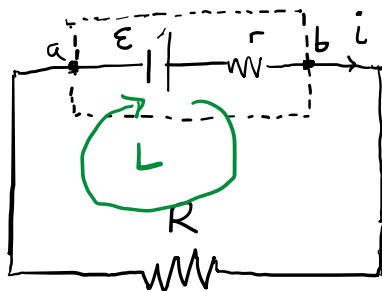Consider the circuit below (which contains a non-ideal battery).



What is the potential difference between points a and b?

LET'S USE KIRCHHOFF'S LOOP RULE.

$$\underline{L}: \quad \epsilon - i r - i R = 0$$

$$\epsilon = i(r + R) \Rightarrow i = \frac{\epsilon}{r + R}.$$

Now, $V_{ab} = iR$ (ALSO $\epsilon - i r \dots$ SAME RESULT)

$$\Rightarrow V_{ab} = \frac{\epsilon R}{r + R}$$