

3-1-2019: Energy Density and RC Circuits

Friday, March 1, 2019 9:06 AM

Let's review from last time...

$$q = CV$$

Capacitors in parallel $C_{eq} = \sum_{i=1}^n C_i$

series $\frac{1}{C_{eq}} = \sum_{i=1}^n \frac{1}{C_i}$

energy of capacitor...

$$U = \frac{q^2}{2C} = \frac{1}{2} qV = \frac{1}{2} CV^2$$

parallel-plate


capacitor: $C = \frac{\epsilon_0 A}{d}$

what about energy density?

$$u = \frac{\frac{1}{2} \left(\frac{\epsilon_0 A}{d} \right) V^2}{Ad} = \frac{1}{2} \epsilon_0 \left(\frac{V}{d} \right)^2 = \frac{1}{2} \epsilon_0 E^2$$

$$u = \frac{U}{\text{Volume}}$$

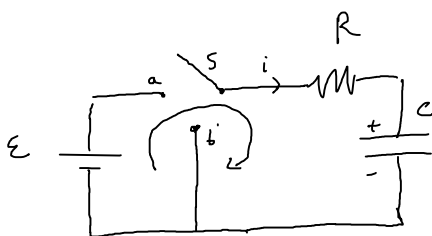Now let's talk about the RC circuit. This circuit involves a capacitor and a resistor, and will be a dynamic system.



initially, no charge on C.

S → position A

$$q(t) \quad V = \frac{q}{C}$$

KLR

$$+\epsilon - iR - V = 0$$

$$\epsilon - iR - \frac{q}{C} = 0$$

REMEMBER, $i = \frac{dq}{dt}$.

$$\epsilon - \frac{dq}{dt} R - \frac{q}{C} = 0$$

$$\Rightarrow \frac{dq}{dt} R = \epsilon - \frac{q}{C} \Rightarrow \frac{dq}{dt} = \frac{\epsilon}{R} - \frac{q}{RC}$$

$$\Rightarrow \frac{dq}{dt} \left(\frac{1}{\frac{\epsilon}{R} - \frac{q}{RC}} \right) = 1$$

Now let's integrate both sides by dt...

$$\int_0^t \left(\frac{1}{\frac{\epsilon}{R} - \frac{q}{RC}} \right) \frac{dq}{dt} dt = \int_0^t dt \Rightarrow \int_0^q \frac{dq}{\frac{\epsilon}{R} - \frac{q}{RC}} = t \Rightarrow -RC \int_{\frac{\epsilon}{R}}^{\frac{\epsilon}{R} - \frac{q}{RC}} \frac{du}{u} = t \Rightarrow -RC \left[\ln|u| \right]_{\frac{\epsilon}{R}}^{\frac{\epsilon}{R} - \frac{q}{RC}} = t$$

$u = \frac{\epsilon}{R} - \frac{q}{RC}$

$$U = \frac{\mathcal{E}}{R} - \frac{q}{RC}$$

$$dU = dq \left(\frac{-1}{RC} \right)$$

$$\Rightarrow \ln \left| \frac{\frac{\mathcal{E}}{R} - \frac{q}{RC}}{\frac{\mathcal{E}}{R}} \right| = -\frac{t}{RC}$$


$$\Rightarrow \ln \left| 1 - \frac{q}{\mathcal{E}C} \right| = -\frac{t}{RC} \Rightarrow 1 - \frac{q}{\mathcal{E}C} = e^{-\frac{t}{RC}} \Rightarrow C\mathcal{E} - q = C\mathcal{E} e^{-\frac{t}{RC}} \Rightarrow -q = C\mathcal{E} (e^{-\frac{t}{RC}} - 1)$$

$$\Rightarrow q(t) = C\mathcal{E} (1 - e^{-\frac{t}{RC}}) \quad \text{charging a capacitor}$$

$$\textcircled{a} t = 0 \dots$$

$$i = \frac{\mathcal{E}}{R}, \quad q = 0, \quad V_C = 0.$$

(C ~ WIRE)

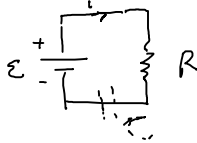


$$i(t) = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-\frac{t}{RC}}$$

$$V_C = \frac{q}{C} = \mathcal{E} (1 - e^{-\frac{t}{RC}})$$

$$\textcircled{b} t = \infty \dots$$

$$i = 0, \quad q = C\mathcal{E}, \quad V_C = \mathcal{E}.$$

(C ~ BROKEN WIRE)

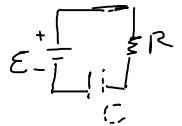

Let's think about the units here... note that the exponent of the $e^{\wedge}()$ needs to be unitless! So,



$$[t] = [R][C] \Rightarrow [s] = [R][C].$$

$$\tau = RC \quad (\text{UNITS, SECONDS})$$


TIME
CONSTANT

$$q = C\mathcal{E} (1 - e^{-\frac{t}{\tau}}) \quad t \rightarrow \tau \Rightarrow q_{\tau} = C\mathcal{E} (1 - e^{-1}) = 0.63 C\mathcal{E}.$$
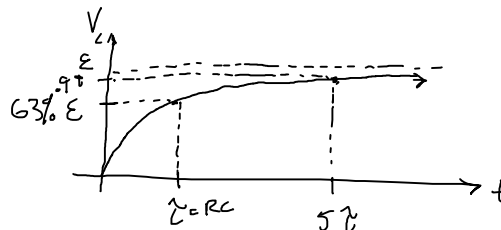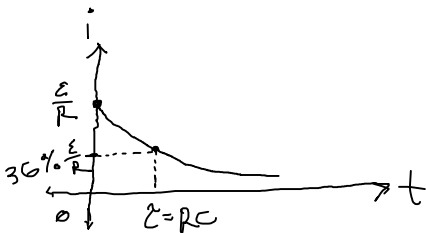
$$t \rightarrow 5\tau \Rightarrow q \sim 99\% \text{ of } C\mathcal{E}.$$




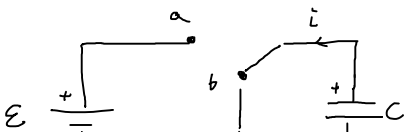Now let's look at what happens in the circuit when we switch to point b instead!



Let's look at our KLR again... notice that our battery is no longer a part of the circuit.

$$-iR - \frac{q}{C} = 0$$

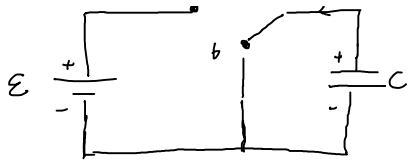

$$\cancel{\epsilon} - iR - \frac{q}{C} = 0$$

$$\frac{dq}{dt} R = -\frac{q}{C}$$

$$\int_0^t \frac{1}{q} \frac{dq}{dt} dt = \int_0^t -\frac{1}{RC} dt$$

$$\int_0^t \frac{dq}{q} = -\frac{t}{RC} \Rightarrow q = q_0 e^{-\frac{t}{RC}} \quad q_0 = C\epsilon$$

$$i = \frac{dq}{dt} = -\frac{q}{RC} e^{-\frac{t}{RC}}$$