

## 2-20-2019: More Ohm's Law and Kirchhoff's Loop Rule

Wednesday, February 20, 2019 9:07 AM

current:  $i = \frac{dq}{dt}$   $\vec{j} = \frac{i}{A}$

$\vec{V}_d = \frac{\vec{j}}{ne}$   $R = \frac{V}{i} (\Omega)$   $\rho = \frac{E}{j} \Rightarrow R = \frac{\rho L}{A}$


Remember that we can only use these equations in an isotropic material (meaning that the resistivity is the same in both directions). If we don't have that, we will get a conductivity tensor.

$\rho = \frac{E}{j}$ ,  $\sigma = \frac{1}{\rho}$   
 ↑                      ↑  
 RESISTIVITY      CONDUCTIVITY

Some materials obey Ohm's law very well, but others do not.

$R = \frac{V}{i}$  — OR —  $\rho = \frac{E}{j}$


$V \propto i$

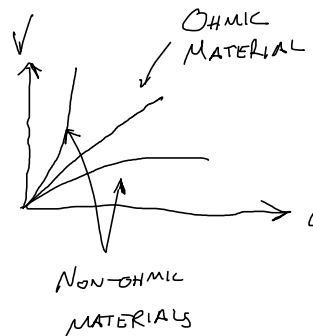

If there isn't a potential across the wire, the electrons will engage in a "random walk" behavior, with a net velocity that is zero.



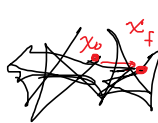However, when there's a potential difference, the electron will move in the preferred direction over time **on average**.



$V_d = \frac{x_f - x_0}{\Delta t} \approx 10^{-5} \text{ m/s}$

$V_{eff} \text{ still } \approx 10^6 \text{ m/s}$

$F = ma = qE \Rightarrow a = \frac{qE}{m} = \frac{eE}{m}$   $\swarrow$  accel. for an  $e^-$ .

$V_d = a \tau = \left(\frac{eE}{m}\right) \tau = \frac{j}{ne} \Rightarrow E = \left[\frac{m}{e^2 n \tau}\right] j$

$$V_d = a \tau = \left( \frac{eE}{m} \right) \tau = \frac{\vec{d}}{ne} \Rightarrow E = \frac{\frac{1}{ne} \tau}{\tau} = \frac{1}{e^2 n \tau} \vec{j}$$

This is the mean-free time.

$\rho = \frac{m}{e^2 n \tau}$

Now let's take a look at how to calculate power in these systems...

$$P = \frac{du}{dt} \quad du = dqV$$



$$= \frac{dqV}{dt} = iV \quad (\text{watt}) \quad (W) ; 1W = 1\left(\frac{J}{s}\right)$$

$$i = \frac{V}{R} \Rightarrow P = \frac{V^2}{R} ; V = iR \Rightarrow P = i^2 R$$

emf: electromotive force


An electromotive force can be generated by anything that is "pumping out charges" such as a generator, a battery, solar panels, etc. Most emf sources are not ideal, which is to say that they do not provide a fixed voltage under all conditions.
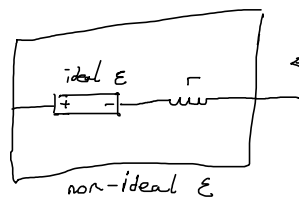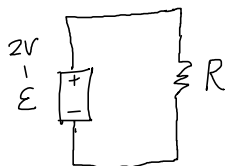
$$\mathcal{E} = \frac{dW}{dq} \quad \left( \frac{J}{C} = V \right)$$



We can think of a non-ideal emf generator as a system that contains an ideal emf and some internal resistance, "r".

A simple circuit example...

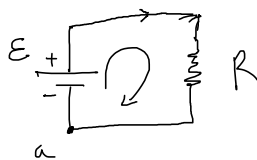

$$R = \frac{\mathcal{E}}{i} \quad i = \frac{\mathcal{E}}{R}$$

Kirchhoff's Loop Rule:

- In a closed loop, the change in potential should be zero.

$$V_a + \mathcal{E} - iR = V_a \Rightarrow \mathcal{E} - iR = 0 \Rightarrow \mathcal{E} = iR$$

Conventions:

emf '+' to '-'

$$\Delta V = -\mathcal{E}$$

'-' to '+'


$$\Delta V = +\mathcal{E}$$

Resistor following  $i$

$$\Delta V = -iR$$

against  $i$ ,

$$\Delta V = +iR$$

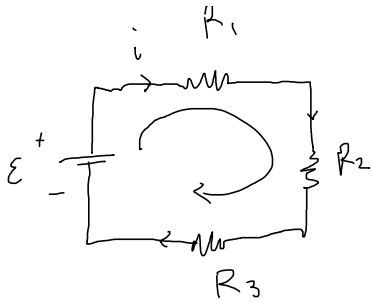

$$\mathcal{E} - iR_1 - iR_2 - iR_3 = 0$$

$$\mathcal{E} = i(R_1 + R_2 + R_3) \Rightarrow \boxed{i = \frac{\mathcal{E}}{R_1 + R_2 + R_3}}$$

$$V = V_1 + V_2 + V_3$$