

### Kirchhoff's Laws and Capacitors

Three capacitors of equal capacitance are arranged in a circuit in parallel with the only other element in the circuit: a battery with emf of 5V. What is the charge on each of the capacitor plates? Suppose one of these capacitors is removed. What happens to the charge on each plate?

$$C_1 = \frac{Q_1}{V_1} = \frac{Q_1}{\mathcal{E}} = C \Rightarrow Q_1 = C\mathcal{E} = 5C$$

$$C_2 = \frac{Q_2}{V_2} = \frac{Q_2}{\mathcal{E}} = C \Rightarrow Q_2 = C\mathcal{E} = 5C$$

$$C_3 = \frac{Q_3}{V_3} = \frac{Q_3}{\mathcal{E}} = C \Rightarrow Q_3 = C\mathcal{E} = 5C$$

$$V = V_1 = V_2 = V_3 = \mathcal{E}$$

$$Q = Q_1 = Q_2 = Q_3 = 5C \quad C = C_1 = C_2 = C_3$$

| IF ONE IS REMOVED,

$$V = V_1 = V_2 = \mathcal{E} \quad C_1 = C_2 = C$$

$$C_1 = \frac{Q_1}{V_1} = \frac{Q_1}{\mathcal{E}} = C \Rightarrow Q_1 = 5C$$

$$C_2 = \frac{Q_2}{V_2} = \frac{Q_2}{\mathcal{E}} = C \Rightarrow Q_2 = 5C$$

SO, THE CHARGE REMAINS THE SAME!

Derive the capacitance of a conducting spherical shell.



$$(r < b).$$

$$E = 0 \Rightarrow V_{ab} = 0$$

$$dr = -ds.$$

$$(r > b).$$

$$E = \frac{q}{4\pi\epsilon_0} \frac{1}{r^2} \hat{r}.$$

$$\Rightarrow V_{b\infty} = - \int_b^{\infty} \vec{E} \cdot d\vec{s} = \int_b^{\infty} E dr$$

$$= \frac{1}{4\pi\epsilon_0} \int_b^{\infty} \frac{dr}{r^2} = \frac{-q}{4\pi\epsilon_0} \left( \frac{1}{r} \right)_b^{\infty}$$

$$= \frac{-q}{4\pi\epsilon_0} \left( \frac{1}{\infty} - \frac{1}{b} \right) = \frac{q}{4\pi\epsilon_0 b}$$

$$C = \frac{Q}{V} = \frac{q}{\frac{q}{4\pi\epsilon_0 b}} = \boxed{4\pi\epsilon_0 b}$$