

Ohm's Law and Kirchhoff's Voltage Rule


Using the observation that electric field in a conductor is proportional to current density (a.k.a. Ohm's Law), can you derive the formula $V=IR$?

Suppose I have two wires:

- one has a radius of $r_1 = 0.100 \text{ m}$, a length of $l_1 = 0.100 \text{ m}$, and a resistivity of $\rho_1 = 5.00 \Omega \cdot \text{m}$.
- a second wire has a radius of $r_2 = 0.200 \text{ m}$, a length of $l_2 = 0.190 \text{ m}$, and a resistivity of $\rho_2 = 5.30 \Omega \cdot \text{m}$.

Which wire has a greater resistivity? Which has a greater resistance?

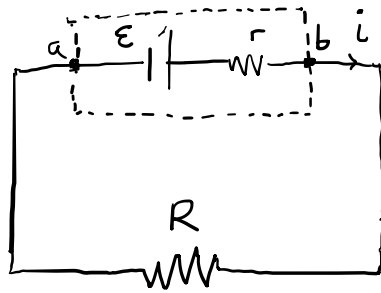Consider the circuit below (which contains a non-ideal battery).



What is the potential difference between points a and b?