

## 2-25-2019: Practice with Circuits and Capacitance


Monday, February 25, 2019 9:01 AM

Let's review calculating some fundamental parameters from circuits that we learned last time...

IN SERIES:  $R_{eq} = \sum_{i=1}^n R_i$

PARALLEL:  $\frac{1}{R_{eq}} = \sum_{i=1}^n \frac{1}{R_i}$ ,  $R_{eq(1,2)} = \frac{R_1 R_2}{R_1 + R_2}$

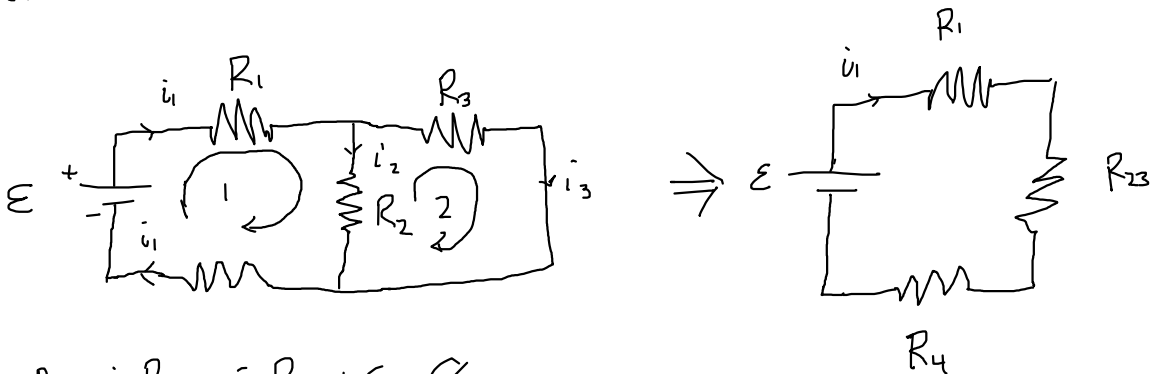ENTERING THE JUNCTION  $\rightarrow i_1 = i_2 + i_3 \leftarrow$  LEAVING THE JUNCTION




①  $-i_1 R_1 - i_2 R_2 - i_1 R_4 + \varepsilon = 0$   
 $\Rightarrow i_2 = \boxed{.18 \text{ A}}$

$R_{23} = \frac{R_2 R_3}{R_2 + R_3} = 12 \Omega$

②  $-i_3 R_3 + i_2 R_2 = 0 \Rightarrow i_3 = \boxed{.12 \text{ A}}$

$i_1 = \frac{\varepsilon}{R_1 + R_{23} + R_4} = \boxed{.30 \text{ A}}$

Now, let's talk about capacitors...

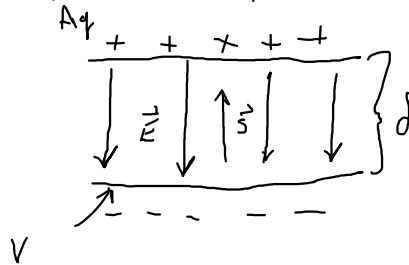


$q = CV \Rightarrow C = \frac{q}{V}$

$q_{net} \neq q$ .  $q_{net} = 0$ .

1 Farad = 1 F = 1  $\frac{C}{V}$

1  $\mu\text{F} = 10^{-6} \text{ F}$

1 pF =  $10^{-12} \text{ F}$

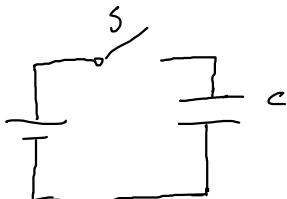

$\oint \vec{E} \cdot d\vec{A} = q_{enc}$

$\varepsilon_0 E A = q_{enc} \Rightarrow E = \frac{q}{\varepsilon_0 A} = \frac{\sigma}{\varepsilon_0} \left( \sigma = \frac{q}{A} \right)$

$$V = - \int \vec{E} \cdot d\vec{s} = Ed = \frac{q}{\epsilon_0 A} d = \frac{d}{\epsilon_0 A} q$$

$$C = \frac{q}{V} = \boxed{\frac{\epsilon_0 A}{d}}$$